

Passive Devices over Frequency

Resistor: $Z_R = R$ for all ω

Capacitor: $Z_C = \frac{1}{j\omega C}$

↳ small freq. = high impedance \leftarrow open

↳ high freq. = low impedance \leftarrow short


Inductor: $Z_L = j\omega L$

↳ small freq. = low impedance \leftarrow short

↳ high freq. = high impedance \leftarrow impedance

Low Pass Filter

Small ω passes through, high ω doesn't

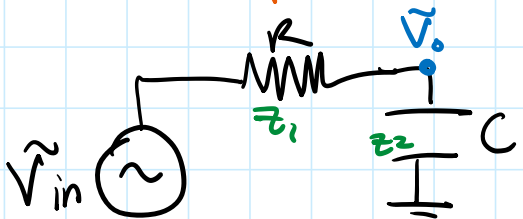

If $\frac{1}{j\omega C}$ is large (small ω), then most of the voltage will be dropped here (after V_o).


If $\frac{1}{j\omega C}$ is small, the voltage will be dropped before V_o .

$Z_1 \gg Z_2$ for small freq.
 $Z_1 \ll Z_2$ for high freq.

$$H(j\omega) \text{ for RC: } \frac{Z_C}{Z_R + Z_C} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{1}{j\omega RC + 1} = \frac{1}{1 + \frac{j\omega}{\omega_c}} = \omega_p$$

High Pass Filter

High ω passes through, small ω doesn't

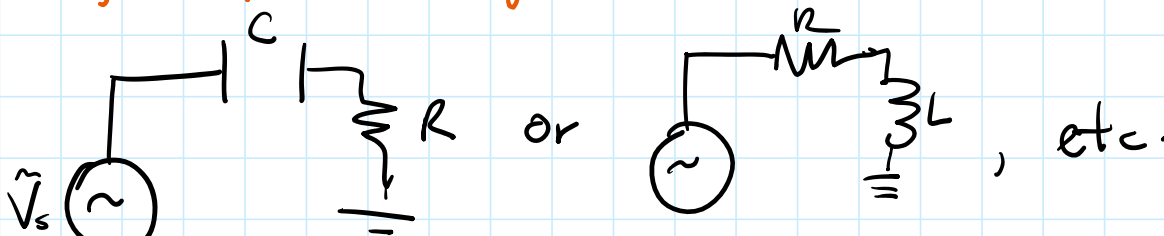




$Z_1 \gg Z_2$ for small freq.
 $Z_1 \ll Z_2$ for high freq.


Bode Plots

$$H(j\omega) = \frac{\underbrace{(j\omega)^n (1 + \frac{j\omega}{\omega_z})}_{\text{zeros}}}{\underbrace{(j\omega)^m (1 + \frac{j\omega}{\omega_p})}_{\text{poles}}}$$


factored transfer function

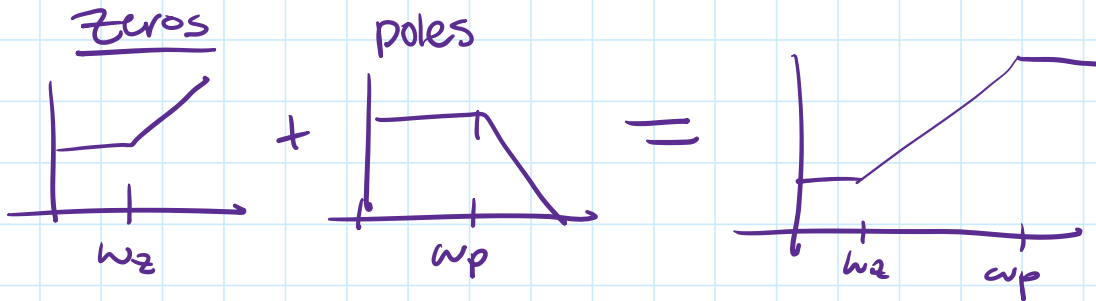


Low pass filter.

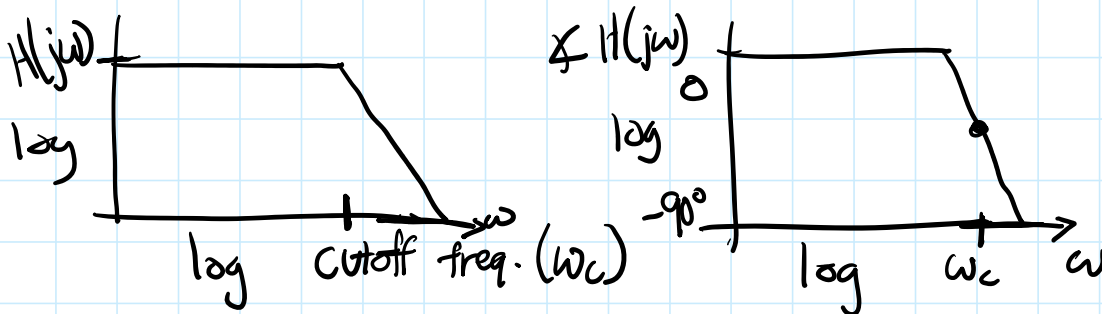

High pass filter:

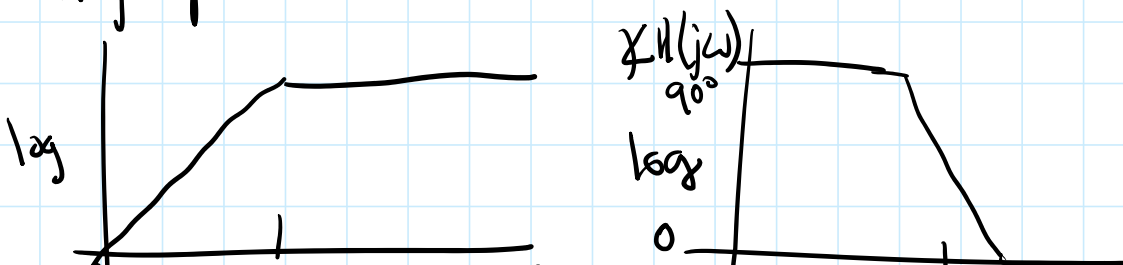


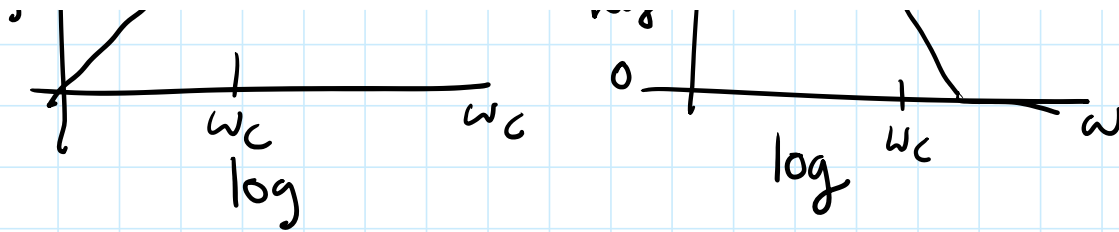

Second Order Filters

→ Filter that has more than one pole/zero

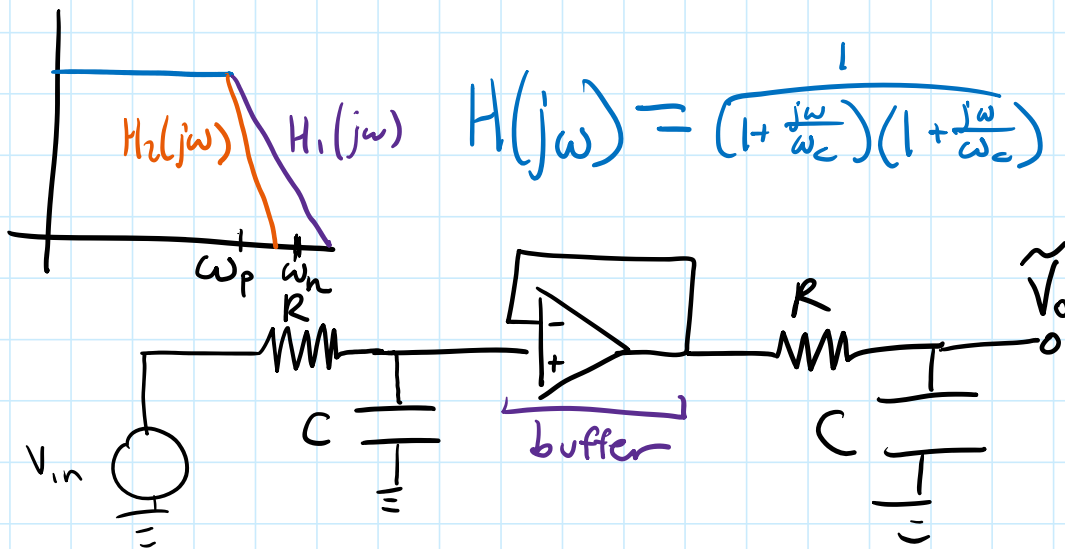
Example: two poles at same value, different transfer functions



Significance:


- multiply j by j to get fully real result
- make band pass filters
- filter out noise that is very similar to actual signal

Band Pass Filter

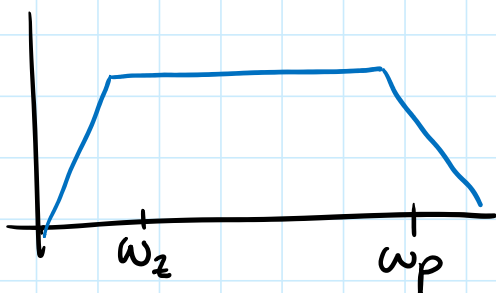


$$H(\omega j) = \frac{\frac{j\omega}{\omega_z}}{\left(1 + \frac{j\omega}{\omega_p}\right)\left(1 + \frac{j\omega}{\omega_z}\right)}$$

→ Resonance

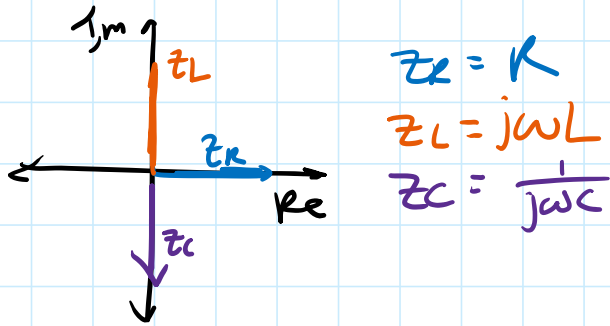

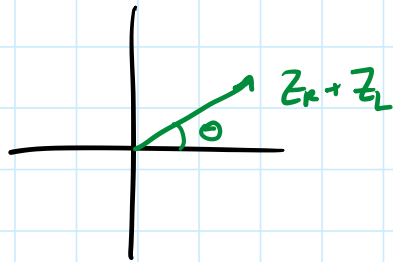* If we take these components in series, the phase will change...




* What if we combine all three?


$$z_R + z_L + z_C = R + j\omega L + \frac{-1}{j\omega C} = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

Resonant Frequency: when $\omega L - \frac{1}{\omega C} = 0$

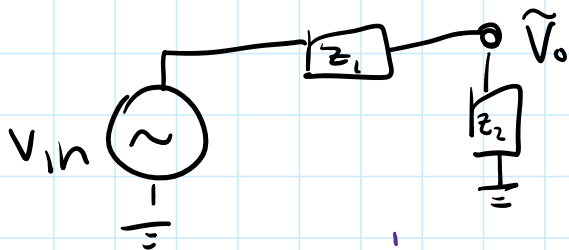Can be used to make a resonant band pass filter.



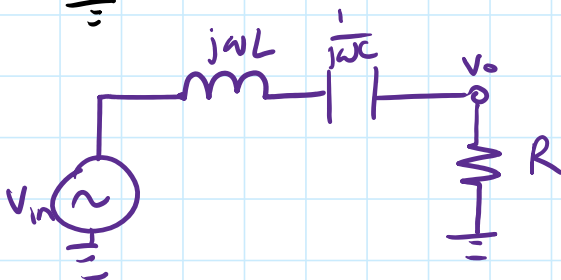
$$\begin{cases}
 H(j\omega) = \frac{z_2}{z_1 + z_2} \\
 z_1 = 0 \text{ if } \omega = \omega_r
 \end{cases}$$





$$H(j\omega) = \frac{R}{R + (j\omega L + \frac{1}{j\omega C})}$$
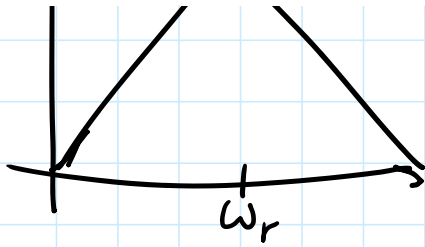
$$\lim_{\omega \rightarrow \infty} H(j\omega) = \lim_{\omega \rightarrow \infty} H(j\omega) = 0$$



Ex: second order filter without loading

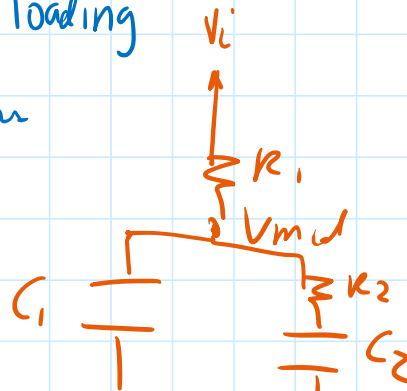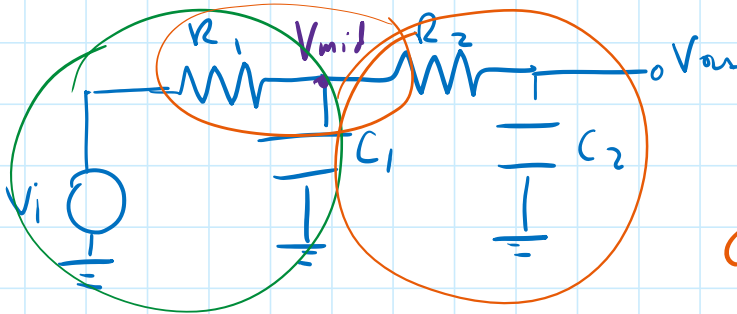

$$H_1(\omega) = \frac{z_{C_1}}{z_{R_1} + z_{C_1}}$$

$$H_2(\omega) = \frac{z_{C_1} \parallel (R_2 \parallel z_{C_2})}{z_{R_1} + (z_{C_1} \parallel (R_2 \parallel z_{C_2}))}$$

← voltage divider of C_1 and $(R_2 \parallel C_2)$ in parallel

$$= \frac{z_{R_2} z_{C_1} + z_{C_1} z_{C_2}}{z_{R_1} z_{C_1} + z_{R_1} z_{R_2} + z_{R_1} z_{C_2} + z_{R_2} z_{C_1} + z_{C_1} z_{C_2}}$$

$$= \frac{1 + j\omega R_2 C_2}{(1 - \omega^2 R_1 R_2 C_1 C_2) + j\omega(R_1 C_1 + R_2 C_2 + R_1 C_2)}$$

=