
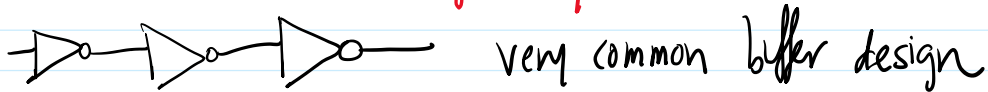


Why do we care about charge delay?

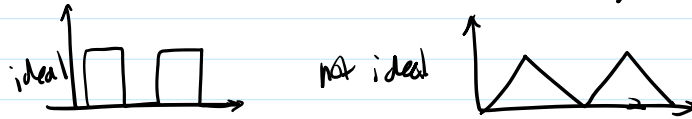


each of these inverters has transistors. each transistor has capacitors.
 → Want to speed up clock speed → capacitor needs to charge faster
 If we set the clock speed, charging will interfere w/ signal.



(delay can be useful for making clocks, larger cap = longer charge time)
 → touchscreens

The Equations:

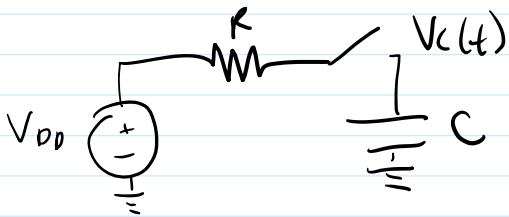

$$I_R = I_C$$

$$C \frac{dV(t)}{dt} = \frac{V_R(t)}{R} = V_{DD} - V_C(t)$$

$$\frac{dV_C(t)}{dt} = \frac{(V_{DD} - V_C(t))}{RC}$$

$$\frac{dV_C(t)}{dt} + \frac{1}{RC} V_C(t) = \frac{V_{DD}}{RC}$$

Differential Equations

$$\frac{d}{dt} x(t) + ax(t) = b$$

Use the solution principle to get

$$x(t) = \underbrace{x_h(t)}_{\text{homogeneous}} + \underbrace{x_p(t)}_{\text{particular}}$$

↳ sol. to $\frac{d}{dt} x(t) + ax(t) = 0$

$$\hookrightarrow \text{sol. to } \frac{d}{dt}x(t) + ax(t) = 0$$

$$\star \text{ eigenfunction: } \frac{d}{dt}x(t) = -ax(t)$$

$$\hookrightarrow x(t) = C_0 e^{-at}$$

$$\text{Initial condition: } x(0) = x_0 = C_0 e^0 = C_0$$

$$\boxed{\frac{d}{dt}x(t) = x_0 e^{-at}}$$

Uniqueness Thm. of Differential Equations

If a function solves a diff eq then it is correct and unique,

- 1) an initial condition $x(t_0)$ exists
- 2) the solution of $x(t)$ is continuous over the desired output range and includes $x(t_0)$

$$\text{Solve } \frac{d}{dt}x(t) + ax(t) = b.$$

$$\frac{d}{dt}x(t) = b - ax(t)$$

$$\int \frac{\frac{d}{dt}x(t)}{x(t) - b/a} = \int -a dt$$

$$\ln|x(t) - b/a| = -at + C$$

$$x(t) = b/a + C' e^{-at}$$

$$x(t) = b/a (x_0 - b/a) e^{-at}$$

\hookrightarrow plug in constants from RC equation to get


$$V_o(t) = \frac{V_{DD}/R_C}{R_C} \left(0 - \frac{V_{DD}}{R_C} \right) e^{-\frac{t}{R_C}}$$

$$V_o(t) = \frac{V_{DD}}{RC} \left(0 - \frac{RC}{RC} \right) e^{-t/RC}$$


$$a = \frac{1}{RC}$$

$$b = \frac{V_{DD}}{RC}$$

$$V_o(t) = V_{DD} (1 - e^{-t/RC})$$

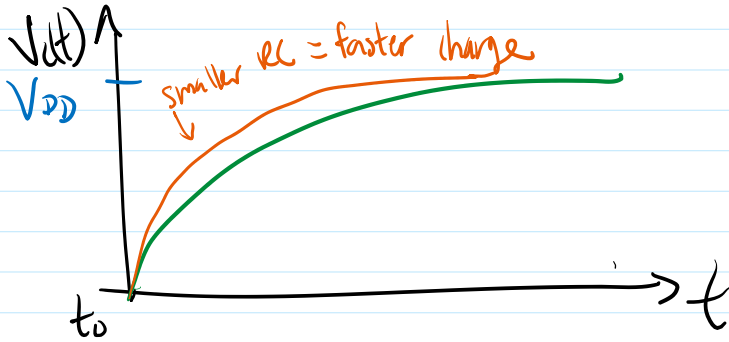



★ RC = time constant

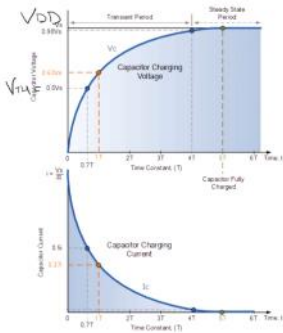

Time Constant	RC Value	Percentage of Maximum Voltage
0.5 time constant	0.5T = 0.5RC	39.3%
0.7 time constant	0.7T = 0.7RC	50.0%
1.0 time constant	1T = RC	63.2%
2.0 time constants	2T = 2RC	86.5%
3.0 time constants	3T = 3RC	95.0%
4.0 time constants	4T = 4RC	98.2%
5.0 time constants	5T = 5RC	99.3%


Application of time constant: ADC

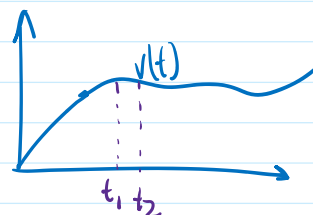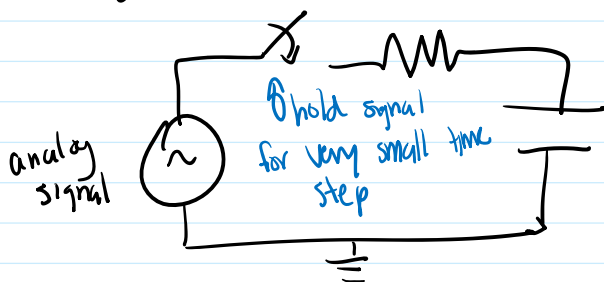An Analog-to-digital converter samples an analog signal at time steps and converts them into digital signals



At t_1 , switch closes
 At t_2 , switch opens and ADC takes voltage

Time Varying Inputs

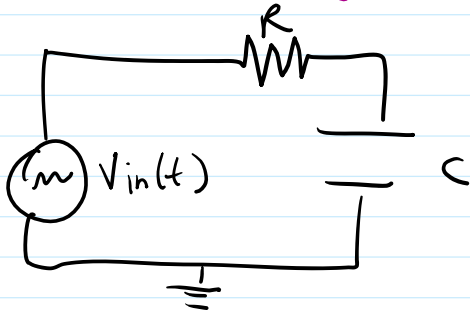

$$\frac{d}{dt} V_o(t) + \frac{1}{RC} V_o(t) = \frac{V_{in}(t)}{RC}$$

Generalized problem: Solve

$$\frac{d}{dt} x(t) + ax(t) = g(t)$$

• Product rule: $\frac{d}{dt} x(t)y(t) = \frac{d}{dt} y(t)x(t) + \frac{d}{dt} x(t)y(t)$

$$= \frac{d}{dt} x(t) + a x(t) = g(t)$$

$$= \frac{d}{dt} x(t)y(t) + ax(t)y(t) = g(t)y(t)$$

$$\frac{d}{dt} x(t)y(t) + \frac{d}{dt} (\int ax(t)y(t)) = g(t)y(t)$$

$$\star \underline{y(t) = e^{at}}$$

Convert to Product Rule.

$$\int \frac{d}{dt} (x(t)y(t)) = \int g(t)y(t) dt$$

$$x(t)e^{at} = \int g(t)e^{at} dt$$

$$x(t) = e^{-at} \int g(t)e^{at} dt$$

homogenous solution

$$\Downarrow \quad (+Ce^{-at})$$

in an RC circuit, $a = \frac{1}{RC}$, $x(t) = V_c(t)$, $g(t) = V_{in}(t)$

in an RC circuit, $a = \frac{1}{RC}$, $x(t) = V_c(t)$, $q(t) = V_{in}(t)$

$$V_c(t) = e^{-\frac{t}{RC}} \int_{t_0}^t \frac{V_{in}(\theta)}{RC} e^{\frac{\theta}{RC}} d\theta$$

Check using a constant: $V_{in}(t) = V_{dd}$, $V_o(0) = 0$

$$V_c(t) = e^{-\frac{t}{RC}} \int_{t_0}^t \frac{V_{dd}}{RC} e^{\frac{\theta}{RC}} d\theta + K e^{-\frac{t}{RC}}$$

$$= e^{-\frac{t}{RC}} \cdot \frac{V_{dd}}{RC} e^{\frac{t}{RC}} \cdot RC + K e^{-\frac{t}{RC}}$$

$$= V_{dd} + K e^{-\frac{t}{RC}}$$

$$V_{dd} + K e^{-\frac{0}{RC}} = 0$$

$$K = -V_{dd}$$

$$V_o(t) = V_{dd} - V_{dd} e^{-\frac{t}{RC}} = V_{dd} (1 - e^{-\frac{t}{RC}})$$

With an exponential $V_{in} = \tilde{V} e^{st}$:

$$V_o(t) = e^{-\frac{t}{RC}} \int \frac{\tilde{V}}{RC} e^{\theta(s+\frac{1}{RC})} + K e^{-\frac{t}{RC}}$$

$$= e^{-\frac{t}{RC}} \frac{1}{(s+\frac{1}{RC})} \frac{\tilde{V}}{RC} e^{t(s+\frac{1}{RC})} + K e^{-\frac{t}{RC}}$$

$$V_o(t) = \frac{\tilde{V}}{sC+1} e^{st} + K e^{-\frac{t}{RC}}$$



Very similar to voltage divider!


$$\frac{\tilde{V}}{sC+1} = \tilde{V} \left(\frac{\frac{1}{sC}}{R+\frac{1}{sC}} \right)$$

with currents: $I_C = \frac{d}{dt} V_c \cdot C = \frac{d}{dt} \tilde{V} e^{st} \cdot C$


$$= s \tilde{V} e^{st} \cdot C$$

So $\frac{\tilde{V}}{I} = \frac{1}{sC} = R_c$

≈

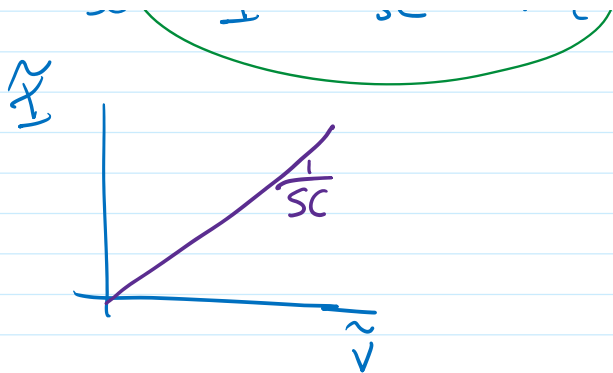

example usage: multiple components

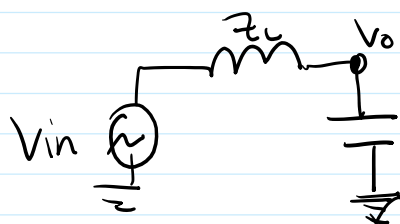

$$\begin{aligned} Z_L &= sL \\ Z_C &= \frac{1}{sC} \\ Z_R &= R \end{aligned}$$

voltage divider
equivalences

$$\begin{aligned} V_o &= V_{in} \frac{Z_C}{Z_C + Z_L} \\ &= V_{in} \frac{\frac{1}{sC}}{\frac{1}{sC} + sL} \end{aligned}$$

Steady State: wait until e^{-t/τ_c} is negligible and $K \approx 0$
so that the exponential $K e^{-t/\tau_c}$ becomes insignificant