
 


## Inverter

 

$V_{in}$	NMOS	PMOS	$V_{out}$
$V_{DD}$	on	off	$V=0, P=0$
0	off	on	$V=V_{DD}, P=0$

## Equations


NMOS:  $V_{cs} \geq V_{in}$   $\leftarrow$  The voltage difference between S

## Equations


NMOS:  $V_{GS} \geq V_{in}$  ← The voltage difference between S and G must be positive.

$$V_{GS} = V_G - V_S$$

Result: current flows from D to S

 


 PMOS:  $V_{SG} = V_S - V_G \geq 0$  ← S has higher voltage, D has lower voltage



$V_{th}$  always  $> 0$

## Single Transistor Inverter

 


i) When  $V_{in} = 0$ ,  $V_{out} = V_{DD}$  (switch open)

ii) When  $V_{in} = V_{DD}$ , switch is on since  $V_{GS} \geq V_{th}$   
 →  $V_{out}$  is connected directly to ground so  $V_{out} = 0V$

 iii) When open,  $P = 0$  since  $I = 0$   
 when closed,  $P = \frac{V_{DD}^2}{R}$

Significance: transistors always consume power when activated  
 Solution: CMOS inverter



### 3 NAND Circuit

Let us consider a NAND logic gate. This circuit implements the boolean function  $\overline{A \cdot B}$ .

 


Figure 6: NAND

$V_{tn}$  and  $V_{tp}$  are the threshold voltages for the NMOS and PMOS transistors, respectively. Assume that  $V_{DD} > V_{tn}$  and  $|V_{tp}| > 0$ .

a) Label the gate, source, and drain nodes for the NMOS and PMOS transistors above.

$V_A$	$V_B$	$N_1$	$N_2$	$P_1$	$P_2$	$V_{out}$
$V_{dd}$	$V_{dd}$	on	on	off	off	0
0	$V_{dd}$	on	off	on	off	$V_{dd}$
$V_{dd}$	0	off	on	off	on	$V_{dd}$
0	0	off	off	on	on	$V_{dd}$